Q3) <u>LEDs And BUTTON</u>

Category: Easy

Make a circuit using arduino, in which we have a button switch and two LEDs, when we press the button one LED glows and another is OFF and when we press it again the LED in OFF state glows and the glowing one goes OFF.